

Unit 4.7: Transfer Functions for Circuit Analysis


AnnotateHighlight

Contents

- [Agenda](#)
- [Transfer Functions for Circuits](#)
- [Examples 14](#)
- [Summary](#)
- [Next time](#)
- [References](#)
- [Matlab Solutions](#)

The preparatory reading for this section is [Chapter 4.4 \[Karris, 2012\]](#) which discusses transfer function models of electrical circuits. We have also adapted content from [3.6 The System Function](#) from [\[Hsu, 2020\]](#).

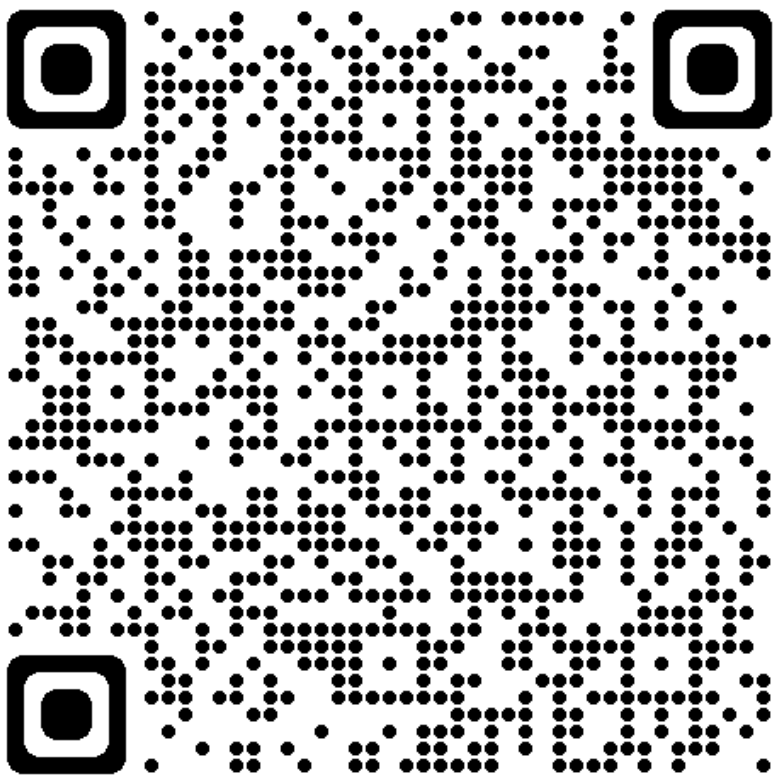Follow along at cpjobling.github.io/eg-150-textbook/laplace_transform/7/tf_for_circuits



Agenda

In this unit, we will explore how transfer functions introduced in [Unit 4.6: Transfer Functions](#) can be applied to the analysis of circuits.

- [Transfer Functions for Circuits](#)
- examples14

```
% Initialize MATLAB
clearvars
cd ../matlab
pwd
format compact

ans =

'/Users/eechris/code/src/github.com/cpjobling/eg-150-
textbook/laplace_transform/matlab'
```

Transfer Functions for Circuits

When doing circuit analysis with components defined in the complex frequency domain, the ratio of the output voltage $V_{\text{out}}(s)$ to the input voltage $V_{\text{in}}(s)$ under zero initial conditions is of great interest.

This ratio is known as the *voltage transfer function* denoted $G_v(s)$:

$$G_v(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)}$$

Similarly, the ratio of the output current $I_{\text{out}}(s)$ to the input current $I_{\text{in}}(s)$ under zero initial conditions, is called the *current transfer function* denoted $G_i(s)$:

$$G_i(s) = \frac{I_{\text{out}}(s)}{I_{\text{in}}(s)}$$

In practice, the current transfer function is rarely used, so we will use the voltage transfer function denoted:

$$G(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)}$$

(examples14)=

Examples 14

We will work through these and demonstrate the MATLAB solutions in class.

Example 14.1

Derive an expression for the transfer function $G(s)$ for the circuit shown in [Fig. 67](#).

In this circuit R_g represents the internal resistance of the applied (voltage) source v_s , and R_L represents the resistance of the load that consists of R_L , L and C .

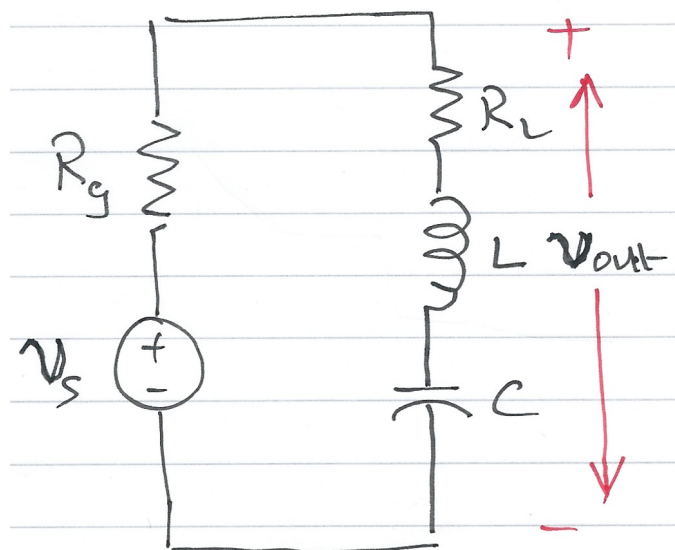


Fig. 67 Circuit for Example 14.1

Sketch of Solution for Example 14.1

- Replace $v_s(t)$, R_g , R_L , L and C by their transformed (*complex frequency*) equivalents: $V_s(s)$, R_g , R_L , sL and $1/(sC)$
- Use the *Voltage Divider Rule* to determine $V_{\text{out}}(s)$ as a function of $V_s(s)$
- Form $G(s)$ by writing down the ratio $V_{\text{out}}(s)/V_s(s)$

Switch to virtual whiteboard in OneNote.

Solve in OneNote

Worked solution for Example 14.1

Pencast: [ex6.pdf](#) - open in Adobe Acrobat Reader.

Answer for Example 14.1

$$G(s) = \frac{V_{\text{out}}(s)}{V_s(s)} = \frac{R_L + sL + 1/sC}{R_g + R_L + sL + 1/sC}.$$

Example 14.2

Compute the transfer function for the op-amp circuit shown in Fig. 68 in terms of the circuit constants R_1 , R_2 , R_3 , C_1 and C_2 .

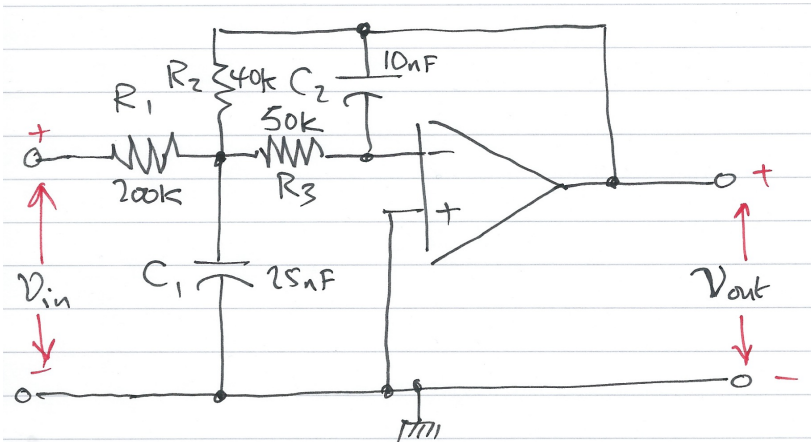


Fig. 68 OpAmp circuit for Example 14.2

Then replace the complex variable s with $j\omega$, and the circuit constants with their numerical values and plot the magnitude

$$|G(j\omega)| = \frac{|V_{\text{out}}(j\omega)|}{|V_{\text{in}}(j\omega)|}$$

versus radian frequency ω rad/s.

Sketch of Solution for Example 14.2

- Replace the components and voltages in the circuit diagram with their complex frequency equivalents
- Use nodal analysis to determine the voltages at the nodes either side of the 50K resistor R_3

Sketch of Solution for Example 14.2 (continued)

- Note that the voltage at the input to the op-amp is a virtual ground
- Solve for $V_{\text{out}}(s)$ as a function of $V_{\text{in}}(s)$
- Form the reciprocal $G(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$

Switch to virtual whiteboard in OneNote.

Solve in OneNote

Answer for Example 14.2

$$G(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = \frac{-1}{R_1 \left((1/R_1 + 1/R_2 + 1/R_3 + sC_1) (sC_2R_3) + 1/R_2 \right)}.$$

(41)

Worked solution for Example 14.2

Pencast: [ex7.pdf](#) - open in Adobe Acrobat Reader.

Sketch of Solution for Example 14.2 (continued)

- Use MATLAB to calculate the component values, then replace s by $j\omega$.
- Compute $|G(j\omega)|$ and plot on log-linear “paper”.

The Matlab Bit

Set up the symbols we will be using. In this case just the Laplace complex frequency s .

```
syms s
```

Now define the values of the components

```
R1 = 200*10^3;  
R2 = 40*10^3;  
R3 = 50*10^3;  
  
C1 = 25*10^(-9);  
C2 = 10*10^(-9);
```

Define the transfer function derived from analysis (Eq. **eg:ex14.2**)

```
den = R1*( (1/R1+ 1/R2 + 1/R3 + s*C1)*(s*R3*C2) + 1/R2)
```

```
den =
```

```
100*s*( (7555786372591433*s)/302231454903657293676544 + 1/20000) + 5
```

Simplify coefficients of s in the denominator. Note **sym2poly** converts a symbolic polynomial with numerical coefficients into a MATLAB polynomial.

```
format long  
denG = sym2poly(den)
```

```
denG =  
0.000002500000000    0.005000000000000    5.000000000000000
```

Now define the denominator

```
numG = -1;
```

Plot the frequency response

For convenience, define coefficients *a* and *b*:


```
a = denG(1);  
b = denG(2);
```

$$G(j\omega) = \frac{-1}{a\omega^2 - jb\omega + 5}$$

```
w = 1:10:10000;  
Gw = -1./(a*w.^2 - j.*b.*w + denG(3));
```

Plot $|G(j\omega)|$ against ω on log-lin “graph paper”.

```
semilogx(w, abs(Gw))  
xlabel('Radian frequency w (rad/s)')  
ylabel('|Vout/Vin|')  
title('Magnitude Vout/Vin vs. Radian Frequency')  
grid
```

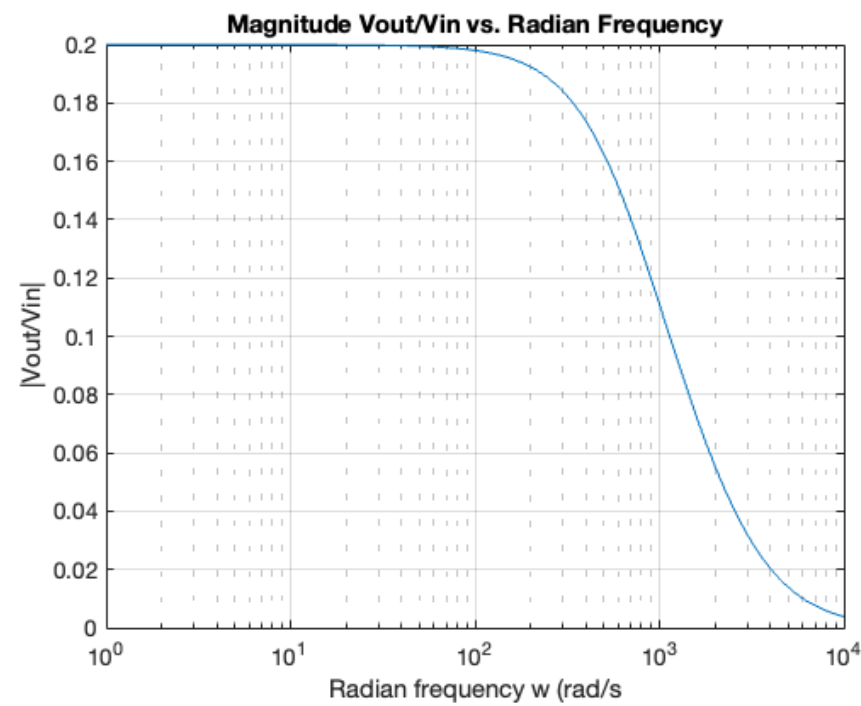

Note that this is a low-pass filter. Sinusoids at low frequencies are passed with a gain of 0.2. For frequencies above around 100 ra/s, the filter starts to reduce the attenuation of the passed signal. At 10,000 rad/s, the attenuation is 1/10 of the attenuation at 1 rad/s.

Summary

In this unit, we will explored how transfer functions introduced in [Unit 4.6: Transfer Functions](#) can be applied to the analysis of circuits.

- [Transfer Functions for Circuits](#)
- examples14

Take Away

The ratio of the output voltage $V_{\text{out}}(s)$ to the input voltage $V_{\text{in}}(s)$ under zero initial conditions is of great interest. We call this ratio the *voltage transfer function*

$$G_v(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)}$$

We can consider other ratios such as the *current transfer function*

$$G_i(s) = \frac{I_{\text{out}}(s)}{I_{\text{in}}(s)}$$

but in practice this is rarely used.

Next time

We explore the facilities provided by other toolboxes in MATLAB, most notably the *Control Systems Toolbox* and the simulation tool Simulink in [Unit 4.8: Computer-Aided Systems Analysis and Simulation](#). We will also look at some of the problems you have studied in **EG-152 Analogue Design** hopefully confirming some of the results you have observed in the lab.

- [Unit 4.8: Computer-Aided Systems Analysis and Simulation](#)

References

[Hsu20] Hwei P. Hsu. *Schaums outlines signals and systems*. McGraw-Hill, New York, NY, 2020. ISBN 9780071634724. Available as an eBook. URL: <https://www.accessengineeringlibrary.com/content/book/9781260454246>.

[Kar12] Steven T. Karris. *Signals and systems with MATLAB computing and Simulink modeling*. Orchard Publishing, Fremont, CA., 2012. ISBN 9781934404232. Library call number: TK5102.9 K37 2012. URL: <https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197>.

Matlab Solutions

For convenience, single script MATLAB solutions to the examples are provided and can be downloaded from the accompanying [MATLAB](#) folder.

- ex:14.2 [[example 14.2.mlx](#)]

By Dr Chris P. Jobling

© Copyright Swansea University (2023).

This page was created by [Dr Chris P. Jobling](#) for [Swansea University](#).